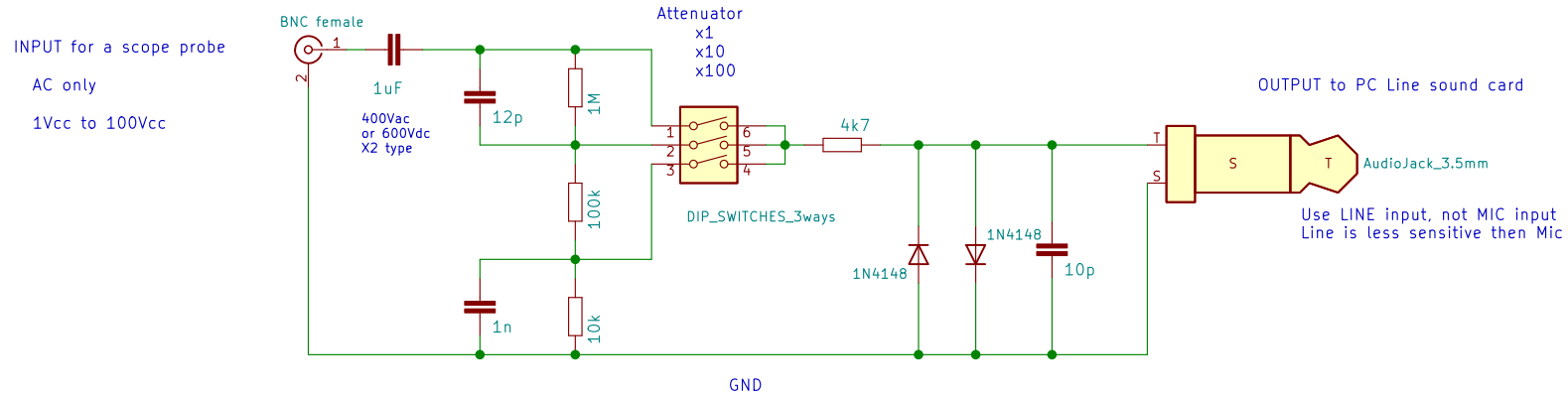



2 exemples of the interface needed to use a PC sound card as an oscilloscope.

Promote battery LAPTOP without connection to main power.


The best one:



The cheapest one:

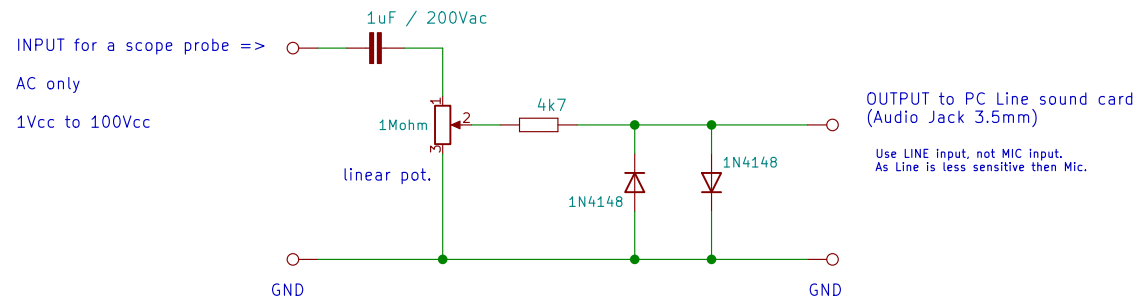

Use this interface with Audacity

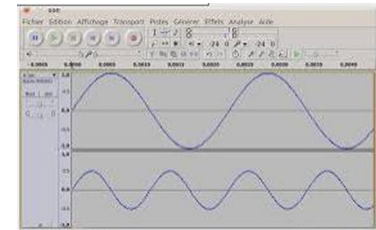

Bear in mind that PC CASE IS CONNECTED TO THE GROUND INPUT.
NEVER connect the ground input of this adapter to a high tension ~
ONLY CONNECT GROUND INPUT TO ANOTHER GROUNDED PART

TITLE: >DRAWING_NAME

Document Number:

TRANSMIC.FR

REV:

1.0

Date: >LAST_DATE_TIME

Sheet: >SHEET

For 2 channels (Line inputs Left and Right) : build two interfaces.